

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	2/ 9 /2024	Batch No:	A2
Faculty Name:	Shivani Deosthale	Roll No:	16010123032
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 5

Title: Flip Flops

Aim and Objective of the Experiment:

To Verify truth table of JK Flip flop using IC 7476 and study conversion of JK FF to D FF and T FF

COs to be achieved:

CO3: Design synchronous and asynchronous sequential circuits.

Tools used:

Trainer kits

Theory:

Flip-flop is the common name given to two-state devices which offer basic memory for sequential logic operations. Flip-flops are heavily used for digital data storage and transfer and are commonly used in banks called "registers" for the storage of binary numerical data.

JK-flip flop: has two inputs, traditionally labeled J and K. IC 7476 is a dual JK master slave flip flop with preset and clear inputs. If J and K are different then the output Q takes the value of J at the next clock edge. If J and K are both low then no change occurs. If J and K are both high at the clock edge, then the output will toggle from one state to the other. It can perform the functions of the set/reset flip-flop and has the advantage that there are no ambiguous states.

D Flip Flop: tracks the input, making transitions with match those of the input D. The D stands for "data"; this flip-flop stores the value that is on the data line. It can be thought of as a basic memory cell. D flip-flop can be made from J-K flip-flop by connecting both inputs through a not gate.


T Flip Flop: T or "toggle" flip-flop changes its output on each clock edge, giving an output which is half the frequency of the signal to the T input. It is useful for constructing binary counters, frequency dividers, and general binary addition devices. It can be made from a J-K flip-flop by tying both of its inputs high.

Implementation Details:


Procedure

- 1) Locate IC 7476 on Digital trainer kit
- 2) Apply various inputs to J & K pins by means of the output on logic output indicator.
- 3) Connect a pulsar switch to the clock input.
- 4) Connect the J&K as D and T flip flop as shown in diagrams and verify the respective truth tables.

Logic Symbol

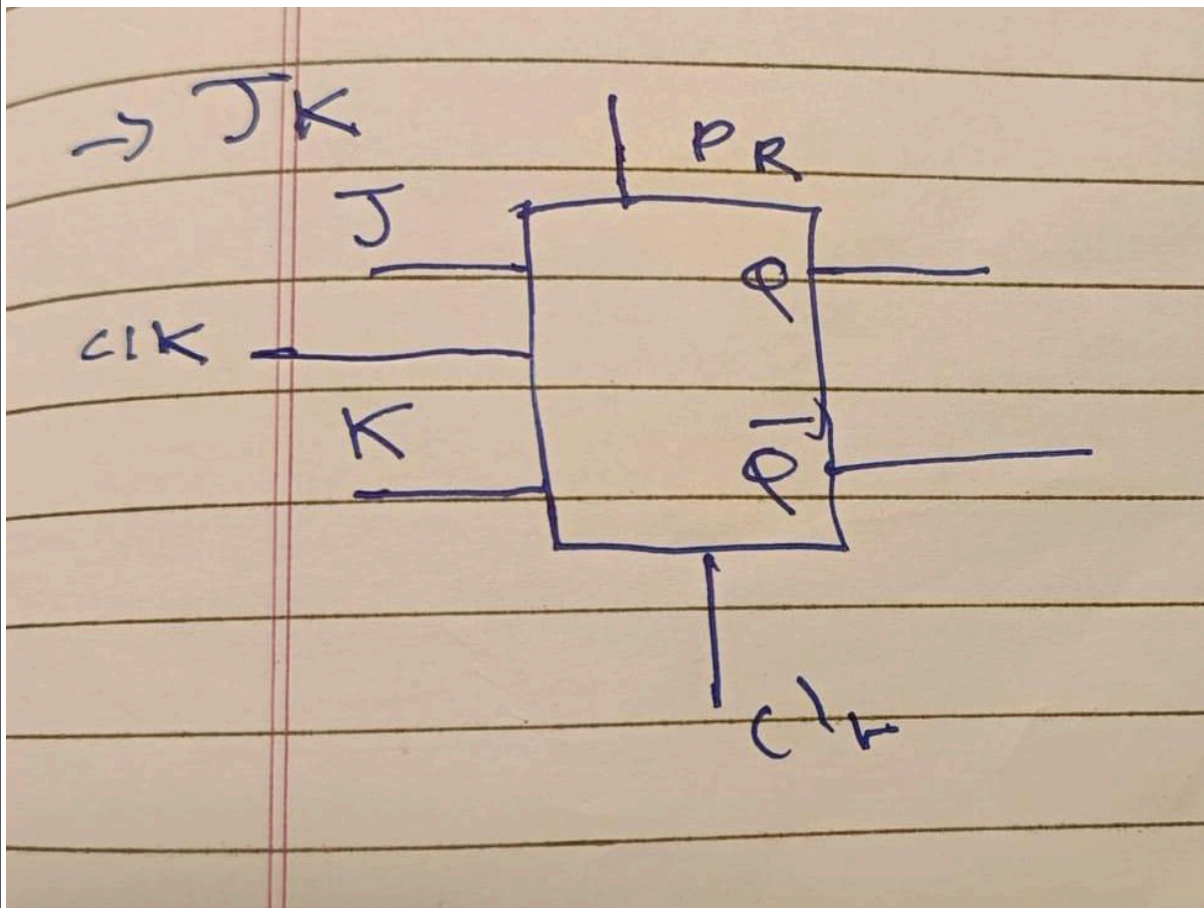

Pin Diagram of IC 7476

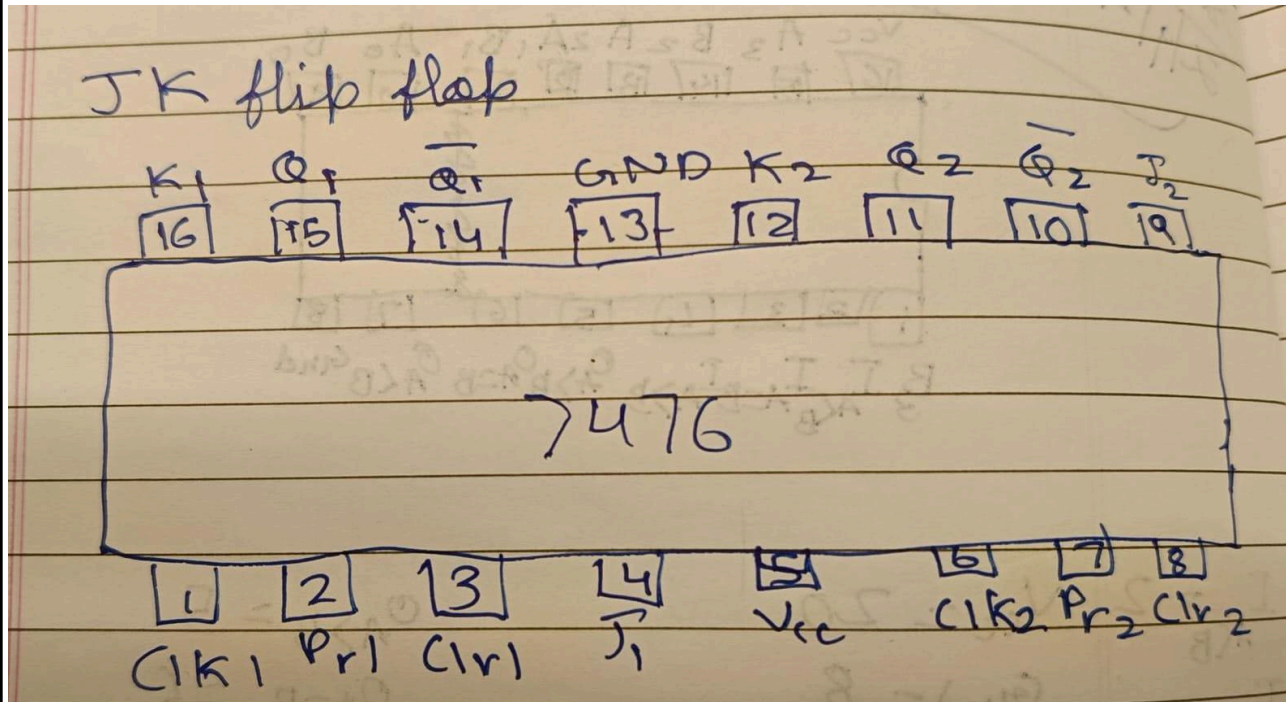


Truth Table of JK FF

CLK	J	K	Pr	Clr	Q	\bar{Q}
0	x	x	x	x	x	x
0	x	x	x	x	x	x
0	x	x	x	x	x	x
0	x	x	x	x	x	x
1	0	0	1	1	Q_n	\bar{Q}_n
1	0	1	1	1	0	1
1	1	0	1	1	1	0
1	1	1	1	1	\bar{Q}_n	Q_n

DATE _____

I/p		O/p
J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

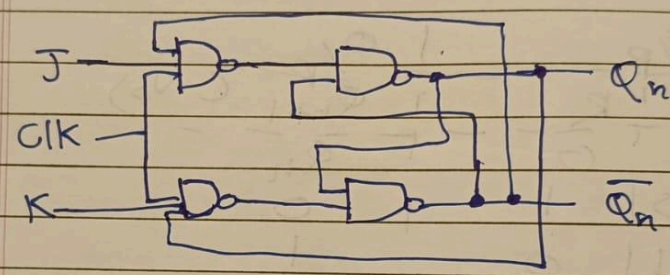


~~Q/K~~
 L
 QnD
 2/9/24

Conversion of FFs

1) JK to D FF

Conversion Diagram

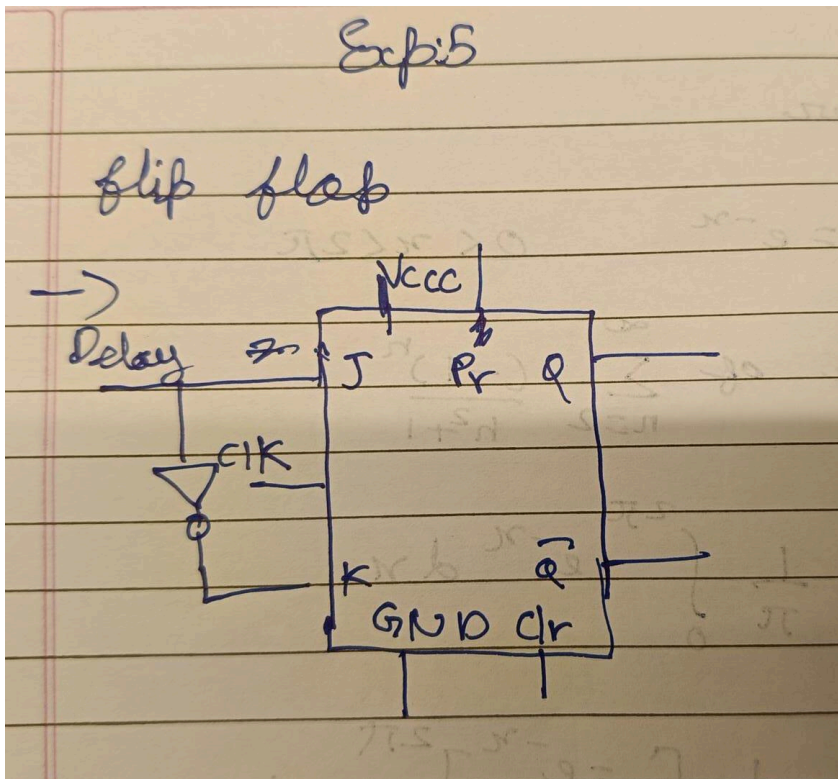


Truth Table of D FF

CLK	D	Q	\bar{Q}
0	x	x	x
1	0	0	1
1	1	1	0

1) JK to T FF

Conversion Diagram

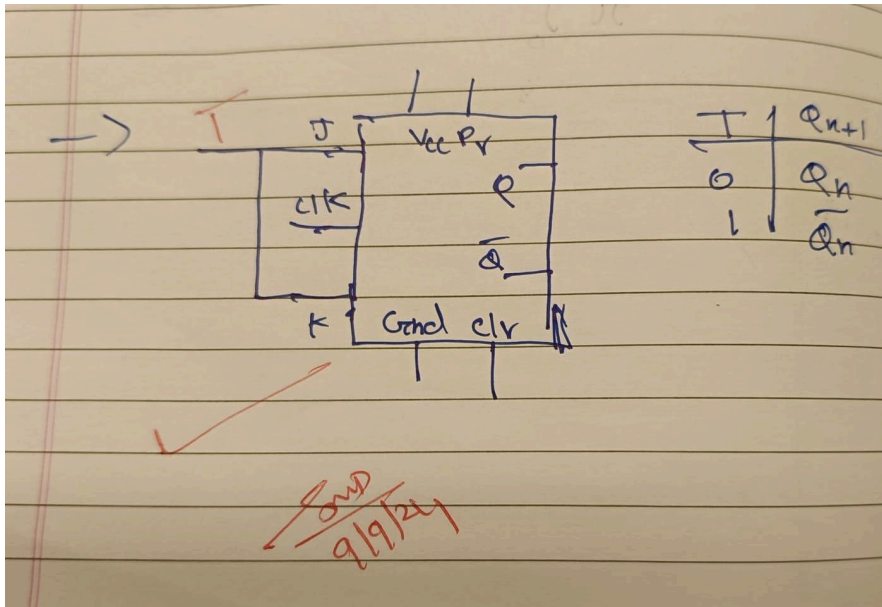

Truth Table of T FF

CLK	T	Q	\bar{Q}
0	x	x	x
1	0	0	Q'
1	1	Q	0

Implementation Details

Procedure:

- 1) Locate the IC 7476 and place the IC on trainer kit.
- 2) Connect VCC and ground to respective pins of IC trainer kit.
- 3) Implement the circuit as shown in the circuit diagram.
- 4) Connect the inputs to the input switches provided in the trainer kit.
- 5) Connect the outputs to the switches of O/P LEDs
- 6) Apply various combinations of inputs according to the truth table and observe the condition of LEDs.
- 7) Note down the corresponding output readings for various combinations of inputs.

Post Lab Subjective/Objective type Questions:

1. How does a JK flip-flop differ from an SR flip-flop in its basic operation?

Ans:

Key Differences Between JK and SR Flip-Flops

1. **Undefined Input Combination:** The JK flip-flop has a defined behavior when both inputs are high (toggle), while the SR flip-flop's behavior is undefined in this state.
2. **Input Functionality:** In a JK flip-flop, both inputs can be used to set or reset the output, while in an SR flip-flop, the S input is used to set and the R input is used to reset.
3. **Versatility:** The JK flip-flop's ability to toggle the output state makes it more versatile and widely used in digital circuits.
4. **Applications:** Both flip-flops are used in various digital circuits, but the JK flip-flop is often preferred due to its flexibility and ease of use.
5. **Design and Analysis:** Characteristic and excitation tables are essential tools for understanding the behavior and designing circuits using both JK and SR flip-flops.

2. What is the use of characteristic and excitation tables?

Ans:

Uses of Characteristic and Excitation Tables

- **Flip-Flop Design:** These tables help in designing sequential circuits by providing a clear understanding of the flip-flop's behavior and the required input conditions.
- **Circuit Analysis:** When analyzing existing circuits, these tables can be used to determine the functionality and operation of flip-flops within the circuit.
- **State Machine Design:** In designing state machines, characteristic and excitation tables are crucial for defining the state transitions and the corresponding input requirements.
- **Fault Diagnosis:** If a circuit is not functioning as expected, these tables can be used to identify potential faults or errors in the flip-flop's operation.
- **Educational Tool:** They serve as a valuable educational aid for understanding the principles and operation of sequential logic circuits.

3. How many flip flops do you require storing the data 1101?


Ans:

To store the 4-bit data "1101", you would need 4 flip-flops. Each flip-flop can store a single bit of data. Since "1101" has 4 bits, you need 4 flip-flops to store the entire value.


4. Virtual Lab for Flipflop. Perform Simulation give feedback.

<https://de-iitr.vlabs.ac.in/exp/truth-tables-flip-flops/simulation.html>


SR flip flop

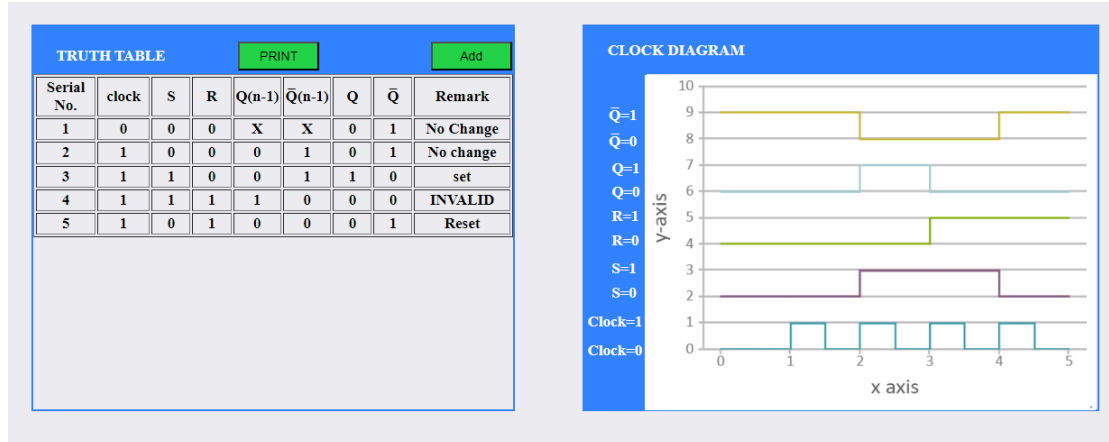


JK flip flop

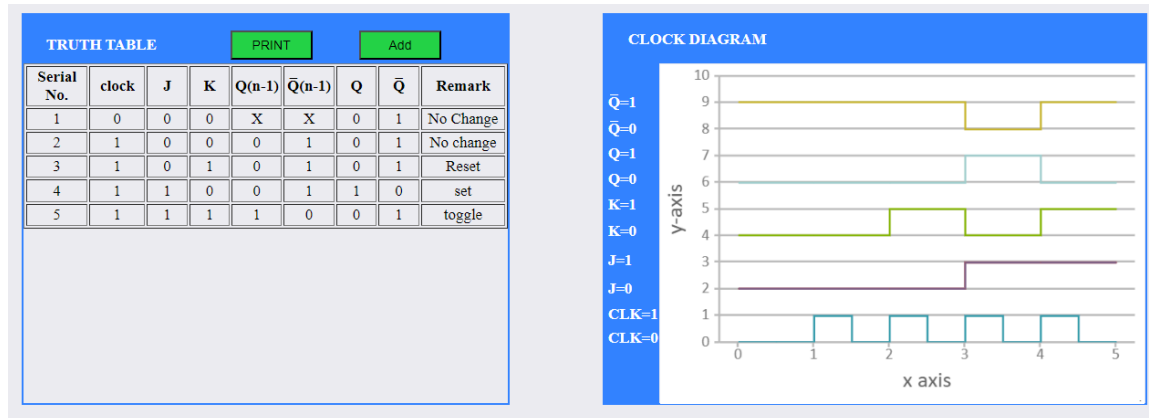

D flip flop

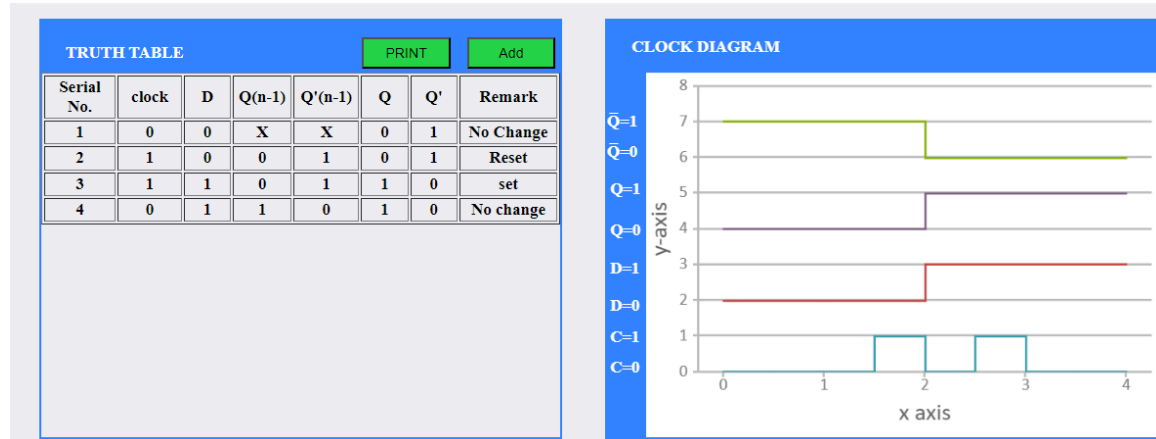

T flip flop

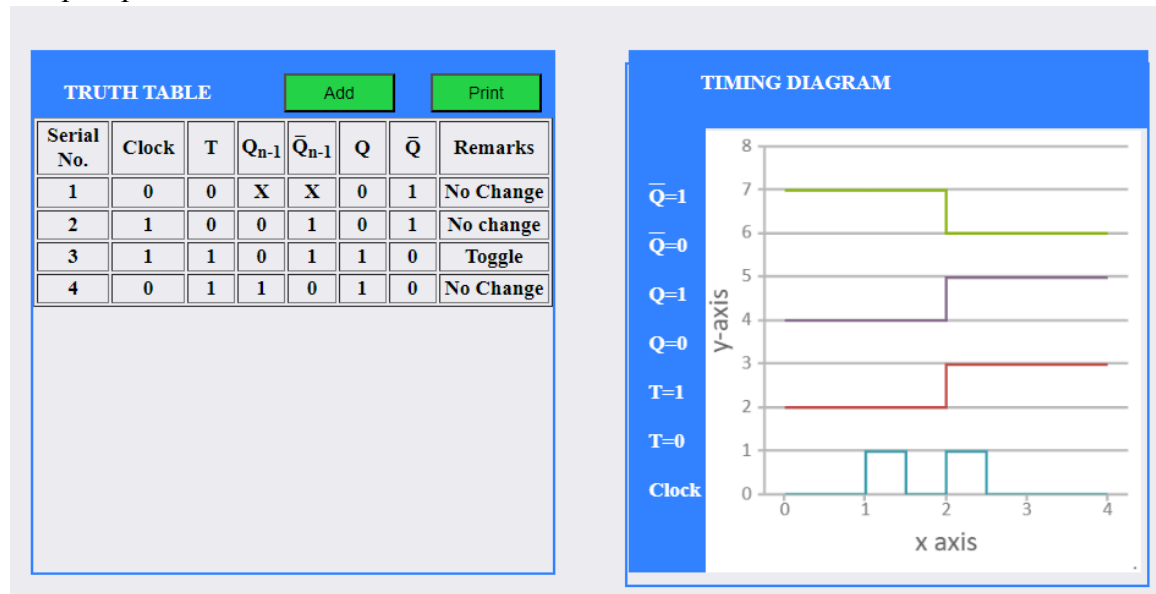

Conclusion:

We successfully verified the truth table of JK Flip flop using IC 7476 and study conversion of JK FF to D FF and T FF

Signature of faculty in-charge with Date: