

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	29/ 07 / 2024	Batch No:	A_2
Faculty Name:		Roll No:	16010123032
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 2

Title: Binary Adders and Subtractors

Aim and Objective of the Experiment:
To implement half and full adder–subtractor using gates and IC 7483

COs to be achieved:
CO2: Use different minimization technique and solve combinational circuits.

Tools used:
Trainer kits

Theory:
<p>Adder: The addition of two binary digits is the most basic operation performed by the digital computer. There are two types of adder:</p> <ul style="list-style-type: none"> ● Half adder ● Full adder <p>Half Adder: Half adder is a combinational logic circuit with two inputs and two outputs. It is the basic building block for the addition of two single-bit numbers.</p> <p>Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi-bit addition is performed. for this purpose, a third input terminal is added and this circuit is to add A, B, and C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.</p> <p>Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer .there are two types of subtractors:</p> <ul style="list-style-type: none"> ● Half subtractor

- Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A,B are 1 bit numbers is referred to as half subtract or .the subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-sub tractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.



IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and C4 respectively.

2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1's complement of that no.

e.g. 2's complement of $+(10)_{10} = 1010$ is

$$\begin{array}{r}
 \text{1C of} \quad \quad \quad 01 \\
 1010 \quad \quad \quad 01 \\
 \quad \quad \quad + \quad 1 \\
 -(10)_{10} \quad \quad 01 \\
 \quad \quad \quad 10
 \end{array}$$

In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.

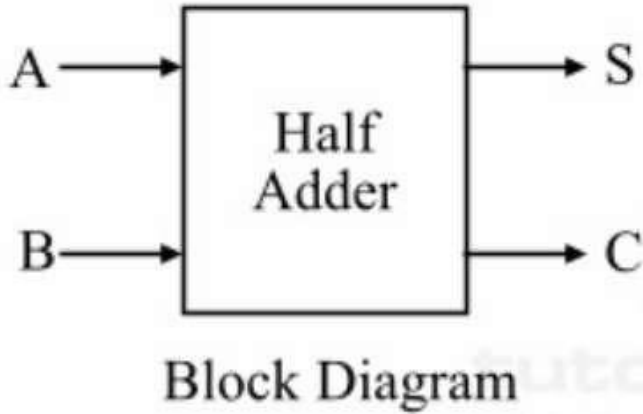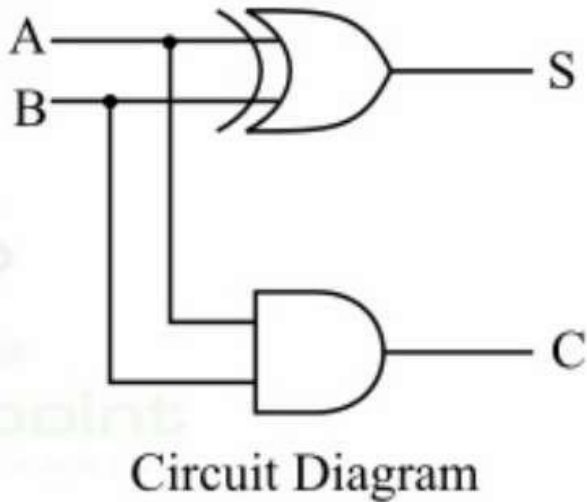Implementation Details:
Half Adder Block Diagram**Half Adder Circuit**

Truth Table for Half Adder


Inputs		Outputs	
A	B	A	B
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

From the truth table (with steps):

$$S = A \oplus B = AB' + A'B$$


$$C = A \cdot B$$

Full Adder Block Diagram

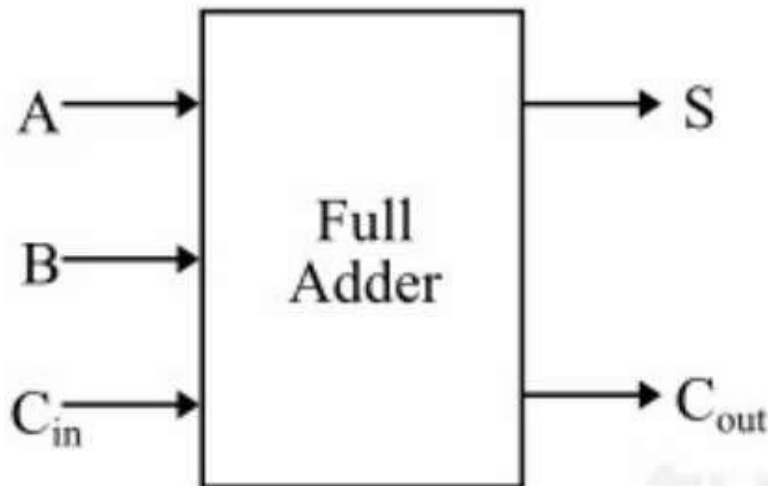

Block Diagram

Full Adder Circuit

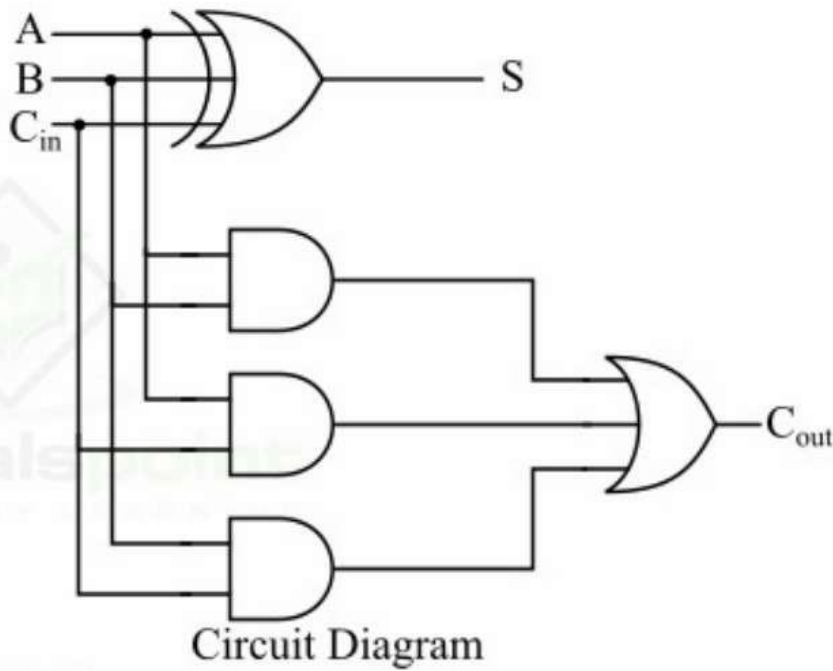

Truth Table for Full Adder


Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

From the truth table (with steps):

$$S = A'B'C_{in} + A'BC_{in}' + AB'C_{in} + ABC_{in}$$


$$C_{out} = AC_{in} + AB + BC_{in}$$

Half Subtractor Block Diagram

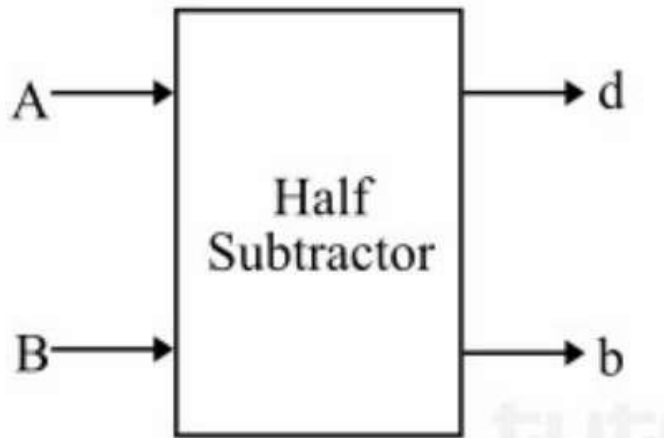

Block Diagram

Half Subtractor Circuit

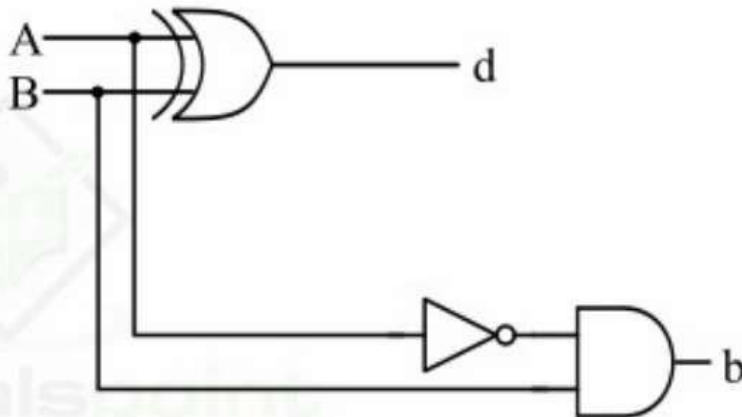

Circuit Diagram

Truth Table for Half Subtractor

DIFFERENCE(D)		BORROW(B ₀)
A	B	


0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

From the truth table (with steps) :

$$\text{Difference}(D) = A'B + AB'$$


$$\text{Borrow}(B) = A'B$$

Full Subtractor Block Diagram

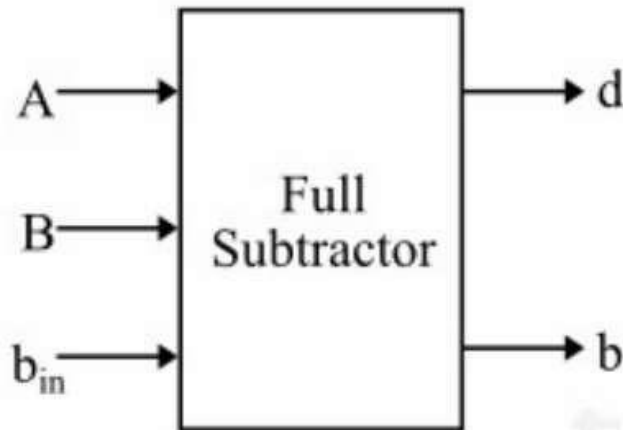

Block Diagram

Full Subtractor Circuit

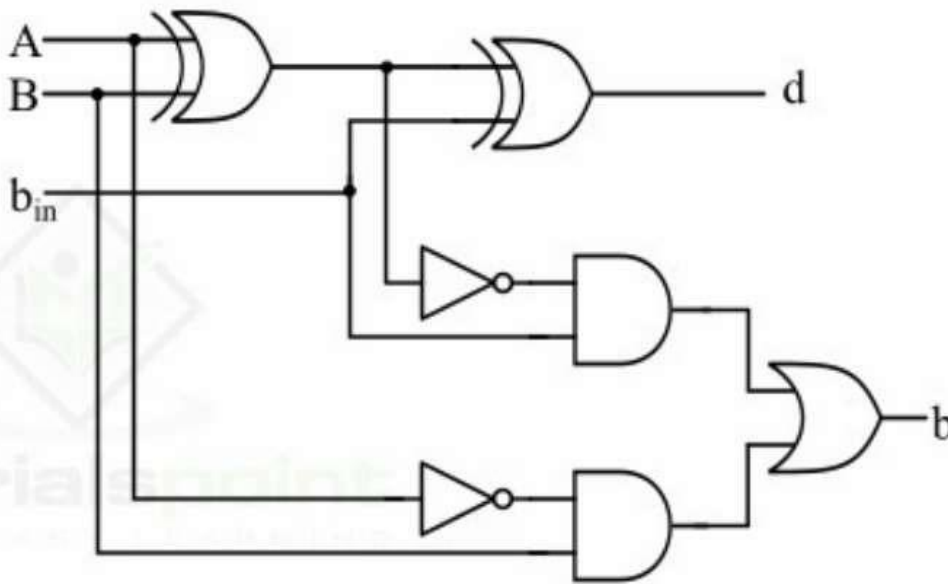

Circuit Diagram

Truth Table for Full subtractor

A	B	B _{IN}	D	BOR _{OUT}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table (with steps):

$$\text{Difference}(D) = A'B'B_{in} + A'BB_{in}' + AB'B_{in}' + ABB_{in}$$

$$\text{BOR}_{out} = A'B + A'B_{in} + BB_{in}$$

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111

2 0010

1'C of 2

1101

+ 1


2'C of 2

1110


0111 + 1110 1

0101


Pin Diagram IC7483

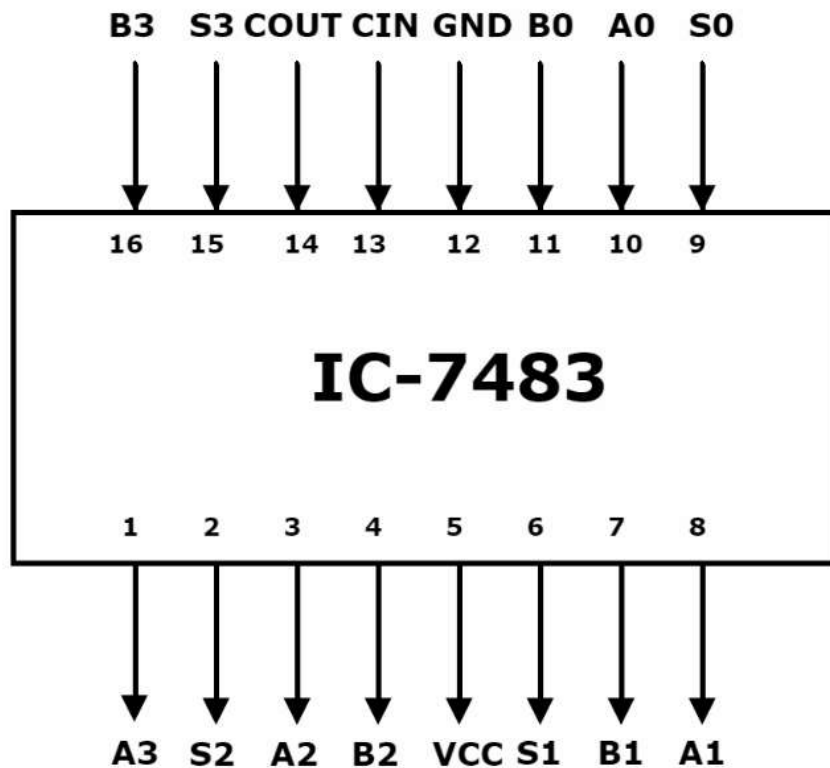

Adder

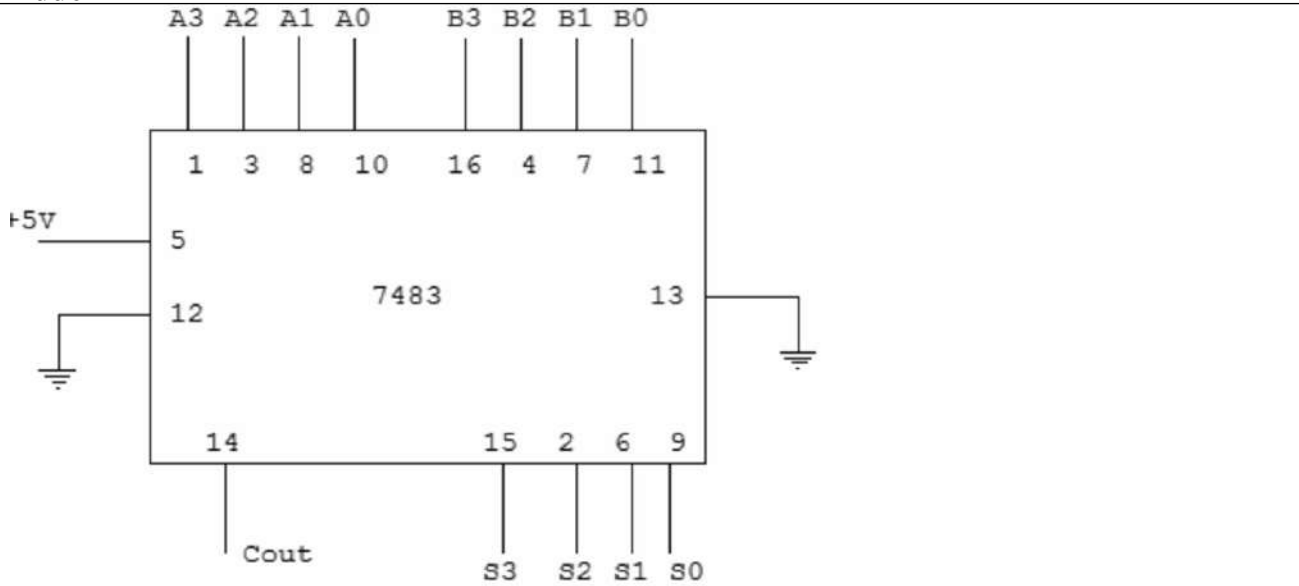

Subtractor

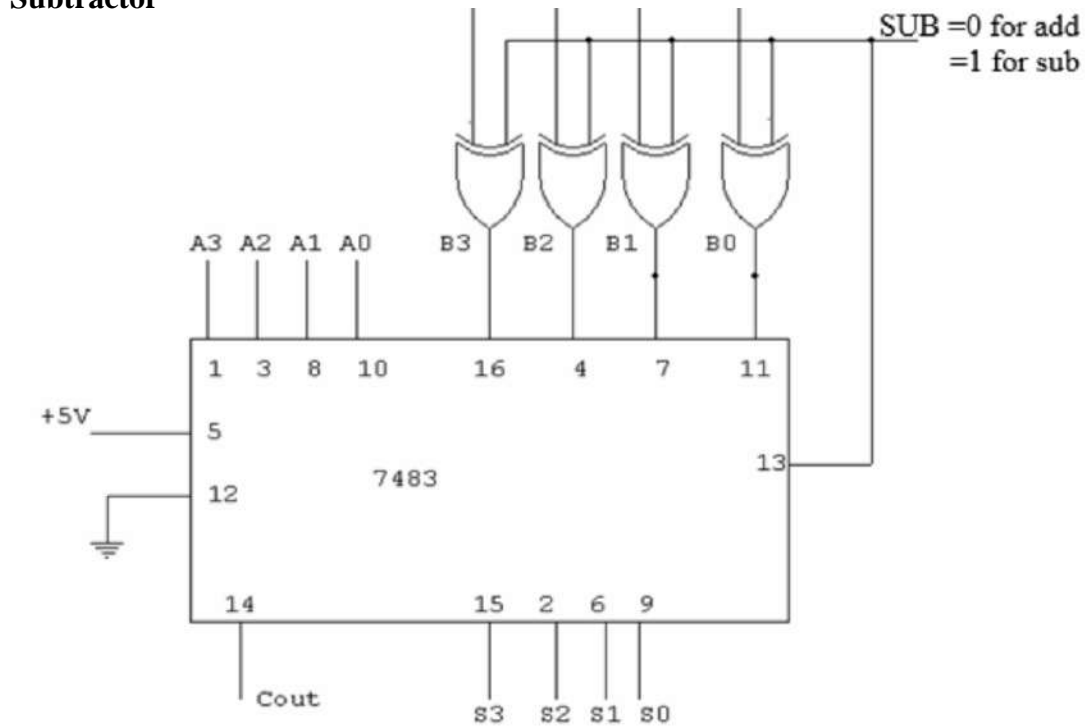

Implementation Details

Procedure:

- 1) Locate the IC 7483 and 4-not gates block on trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to Co so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.

Lab work:

Binary Adder Subtractor Date: / /

Half adder


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B}$$

$$= A \oplus B$$


$$C = AB$$

Imp
24/12

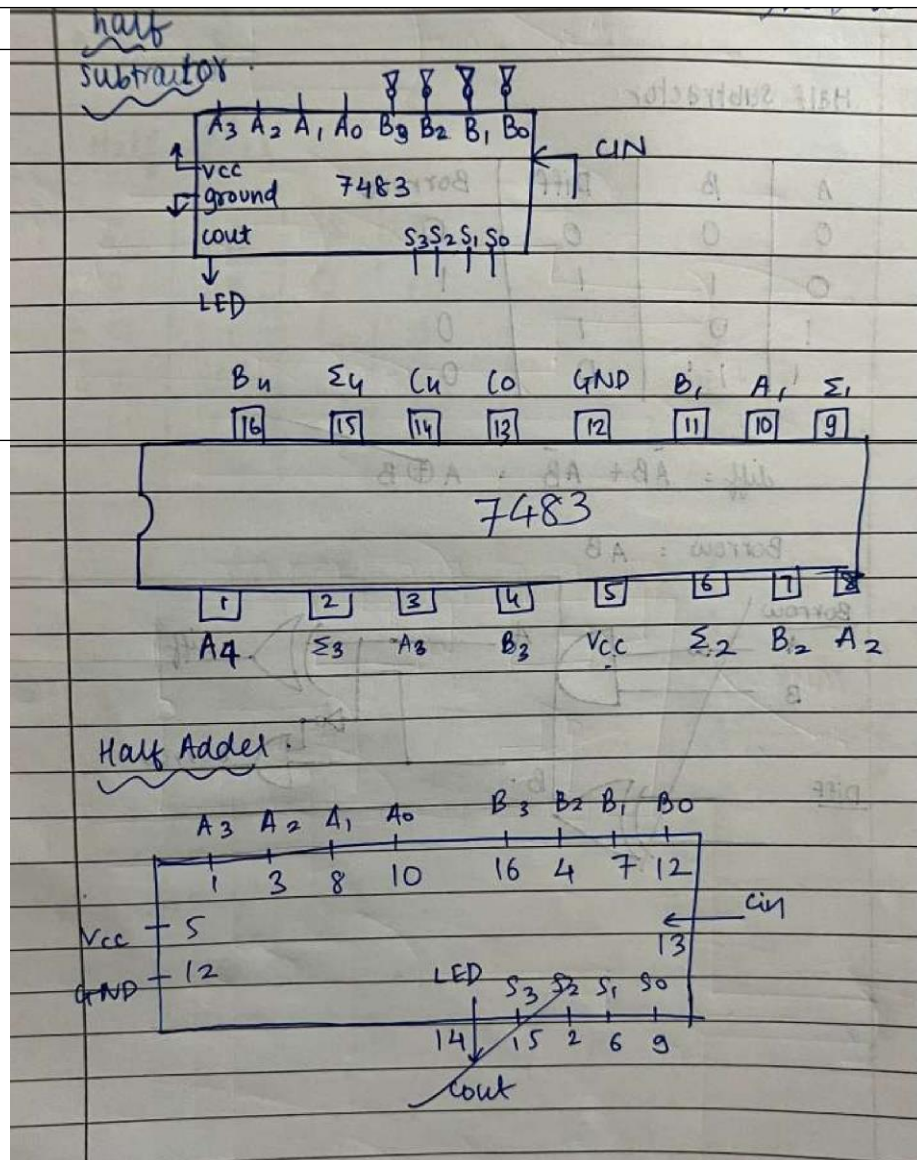

Post Lab Subjective/Objective type Questions:

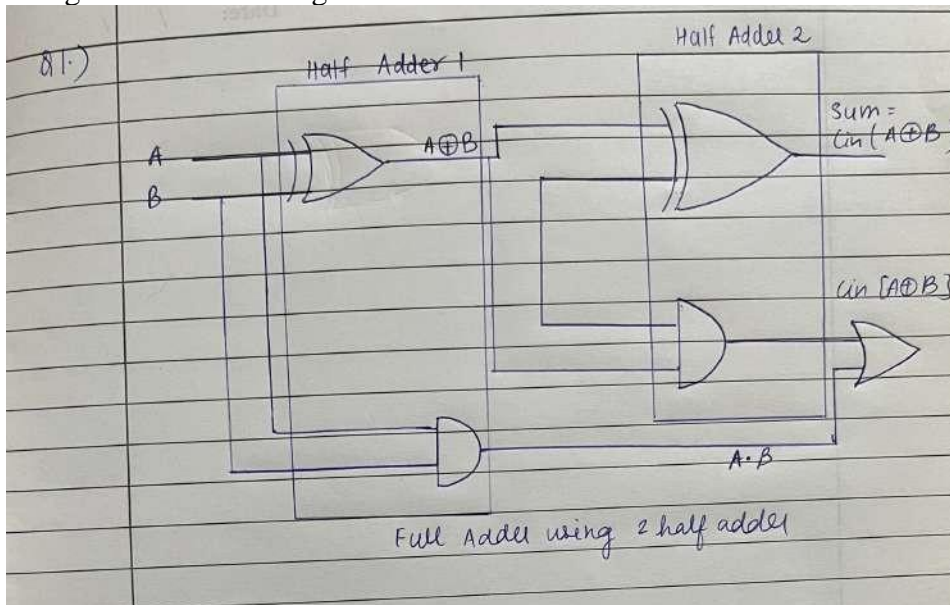1. Design a full adder using two half adders.



2. Perform the following Binary subtraction with the help of appropriate ICs:

a. 6-4 b. 5-8 c. 7-9

Q2.) a) 6-4

$$\begin{array}{r}
 6 = 0110, 4 = 0100 \\
 \sim 4 \text{ [2's complement]} \\
 \begin{array}{r}
 1011 \\
 +1 \\
 \hline
 1100
 \end{array} \\
 \text{adding :- } 0110 + 1100 \\
 = 10010 \\
 \Rightarrow 0010
 \end{array}$$

b) 5-8

$$\begin{array}{r}
 5 = 0101, 8 = 1000, \sim 8 = 0111 \text{ [2's complement]} \\
 \begin{array}{r}
 0111 \\
 +1 \\
 \hline
 1000
 \end{array} \\
 0101 + 1000 \Rightarrow 1101
 \end{array}$$

c) 7-9

$$\begin{array}{r}
 7 = 0111, 9 = 1001, \sim 9 = 0110 \text{ [2's complement]} \\
 \text{adding 1} \Rightarrow 0110 \\
 +1 \\
 \hline
 0111 \\
 \text{now, } 0111 + 0111 \Rightarrow 1110
 \end{array}$$

Conclusion:

We learnt how to successfully implement half and full adder subtractor using gates and IC 7483

Signature of faculty in-charge with Date: